

Lab 4

November 9, 2022

1 Design of a Stepped impedance low-pass filter

1.1 SPECS

- **Maximally Flat**
- Stepped Impedance:
 - $Z_{Low} = 10\Omega$
 - $Z_{High} = 150\Omega$
- Substrate:
 - GIL Technologies GML-1000
 - * $H = 0.762$
 - * $E_r = 3.2$
 - * $\tan_d = 0.003$
- Order of the Filter: 7^{nth}
- Cut-off Frequency: $f_c = 2.0\text{ GHz}$

$$\left| \frac{w}{w_c} \right| - 1 = 0.1N, \quad N = 7 \quad \text{e} \quad w_c = 2 \cdot \pi \cdot 2\text{ GHz}$$

$$\frac{w}{2 \cdot \pi \cdot 2\text{ GHz}} = 0.7 + 1$$

$$w = 3.4\text{ GHz}$$

```
[ ]: !pip install numpy
import numpy as np
z_high = 150
z_low = 10
H = 0.762
E_r = 3.2
tan_d = 0.003
n = 7
f_c = 2e9
w_c = f_c * 2 * np.pi
R_0 = 50
lightspeed = 3e8 #approximation in vacuum should be changed based on substrate
wavelength = lightspeed/ f_c
```

```
[3]: attenuation_w = ((n/10)+1)*w_c #Quando a atenuação e maior que 20dB
      attenuation_f = ((n/10)+1)*f_c #Quando a atenuação e maior que 20dB

      print(f"Freq Attenuation is more than 20dB: {attenuation_f:e} Hz")
      print(f"                : {attenuation_w:e} rad/s")
```

```
Freq Attenuation is more than 20dB: 3.400000e+09 Hz
                : 2.136283e+10 rad/s
```

Since our filter is maximally flat we will use the values from the table provided in slide 17 of *Microwave Filter Design 2*

N	g_0	g_1	g_2	g_3	g_4	g_5	g_6	g_7	g_8
...
7	1.0000	0.4450	1.2470	1.8019	2.0000	1.8019	1.2470	0.4450	1.0000

```
[4]: g_list = [1.0000, 0.4450, 1.2470, 1.8019, 2.0000, 1.8019, 1.2470, 0.4450, 1.
      ↪0000]
      C_list = []
      L_list = []
      i = 0
      for g in g_list:
          if(i <= 0 or i==n+1):
              print(" ")
              #print("Do Nothing")
          elif(i % 2 == 0 and i > 0):
              #print("par")
              L_list.append((R_0*g)/w_c)
          elif(i % 2 == 1 and i > 0):
              #print("impar")
              C_list.append(g/(R_0*w_c))
              #print(g)
              #print(f"i={i}")
              i+=1

      i = 1
      for c in C_list:
          print(f"C{i} = {c:.3e} F")
          i+=1
      i=1
      print(" ")
      for l in L_list:
          print(f"L{i} = {l:.3e} H")
          i+=1
      print(" ")
      beta = (2*np.pi)/wavelength
```

```

print(f"{beta = :.3f}")
print(f"{wavelength = :.3f}")
microstrip_l_list = []
microstrip_betal_list = []
i = 0
for g in g_list:
    if(i % 2 == 0 and i >= 1 and i <= n):
        #print(f"Bobine")
        microstrip_l_list.append(((g*R_0)/z_high)/beta)
        microstrip_betal_list.append((g*R_0)/z_high)
    if(i % 2 == 1 and i >= 1 and i <= n):
        #print("Condensador")
        microstrip_l_list.append((g*z_low)/R_0/beta)
        microstrip_betal_list.append((g*z_low)/R_0)
    i+=1

# Speed of wave in substrate is needed for this calculation
#i=1
#print(" ")
#for l in microstrip_l_list:
#    print(f"Lengh {i} = {l:.3e} m")
#    i+=1

i=1
print(" ")
for l in microstrip_betal_list:
    if(i % 2 == 1): string = f"Capacitor {i}  Z_0={z_low} "
    else: string = f"Inductor {i}  Z_0={z_high}"
    print(f"{string} Angle = {l:.3f} rads or {l * (180/np.pi):.3f} degrees")
    i+=1

```

C1 = 7.082e-13 F
C2 = 2.868e-12 F
C3 = 2.868e-12 F
C4 = 7.082e-13 F

L1 = 4.962e-09 H
L2 = 7.958e-09 H
L3 = 4.962e-09 H

beta = 41.888
wavelength = 0.150

Capacitor 1 Z_0=10 Angle = 0.089 rads or 5.099 degrees
Inductor 2 Z_0=150 Angle = 0.416 rads or 23.816 degrees

Capacitor 3 $Z_0=10$ Angle = 0.360 rads or 20.648 degrees
 Inductor 4 $Z_0=150$ Angle = 0.667 rads or 38.197 degrees
 Capacitor 5 $Z_0=10$ Angle = 0.360 rads or 20.648 degrees
 Inductor 6 $Z_0=150$ Angle = 0.416 rads or 23.816 degrees
 Capacitor 7 $Z_0=10$ Angle = 0.089 rads or 5.099 degrees

```
[ ]: !pip install scikit-rf
      !pip install matplotlib
```

```
[8]: #Plot VNA Result

import skrf as rf
ntwk = rf.Network('data/filtro SI 2GHz-ERF.s2p')
s = ntwk.s
%matplotlib inline
from pylab import *
rf.stylelty()
ntwk.plot_s_db()
```

